 



# Simple Logic



# AND Truth Table

AND	0	1
0	0	0
1	0	1

 - 0 AND 0 is 0 (a false statement AND a false statement is a false combination)
- 0 AND 1 is 0 (a false statement AND a true statement is a false combination)
- 1 AND 0 is 0 (a true statement AND a false statement is a false combination)
- 1 AND 1 is 1 (a true statement AND a true statement is a true combination)




# OR Truth Table

Inclusive OR

OR	0	1
0	0	1
1	1	1

 - 0 OR 0 is 0 (a false statement OR a false statement is a false combination)
- 0 OR 1 is 1 (a false statement OR a true statement is a true combination)
- 1 OR 0 is 1 (a true statement OR a false statement is a true combination)
- 1 OR 1 is 1 (a true statement OR a true statement is a true combination)



# XOR Truth Table

Exclusive OR


XOR	0	1
0	0	1
1	1	0

0 XOR 0 is 0 (a false statement XOR a false statement is a false combination.  
XOR and OR are the same for these inputs.)

0 XOR 1 is 1 (a false statement XOR a true statement is a true combination.  
XOR and OR are the same for these inputs.)

1 XOR 0 is 1 (a true statement XOR a false statement is a true combination.  
XOR and OR are the same for these inputs.)

 1 XOR 1 is 0 (a true statement XOR a true statement is a false combination,  
because XOR excludes both statements being true)




# NOT Truth Table

NOT

0	1
1	0

NOT 0 is 1 (the negative of a false statement is a true statement)

 NOT 1 is 0 (the negative of a true statement is a false statement)



# NAND Truth Table


NAND	0	1
0	1	1
1	1	0

0 NAND 0 is 1 (false AND false is false, which is negated to true)

0 NAND 1 is 1 (false AND true is false, which is negated to true)

1 NAND 0 is 1 (true AND false is false, which is negated to true)

 1 NAND 1 is 0 (true AND true is true, which is negated to false)




# NOR Truth Table

NOR	0	1
0	1	0
1	0	0


- 0 NOR 0 is 1 (false OR false is false, which is negated to true)
- 0 NOR 1 is 0 (false OR true is true, which is negated to false)
- 1 NOR 0 is 0 (true OR false is true, which is negated to false)
- 1 NOR 1 is 0 (true OR true is true, which is negated to false)

# Logic Gate Implementation


## AND Gate

 

 
open AND open is open  
 $0 \text{ AND } 0 = 0$



 closed AND open is open  
 $1 \text{ AND } 0 = 0$





 open AND closed is open  
 $0 \text{ AND } 1 = 0$




closed AND closed is closed  
 $1 \text{ AND } 1 = 1$


## OR Gate

  

 
open OR open is open  
 $0 \text{ OR } 0 = 0$



 closed OR open is closed  
 $1 \text{ OR } 0 = 1$



 open OR closed is closed  
 $0 \text{ OR } 1 = 1$



closed OR closed is closed  
 $1 \text{ OR } 1 = 1$

## NOT Gate



NOT closed is open  
 $\text{NOT } 1 = 0$







NOT open is closed  
 $\text{NOT } 0 = 1$



# Logic Gate Implementation


To make a computer, all you need is Memorial Stadium for an afternoon, a few thousand chairs, a few thousand undergraduates, one pizza for each three undergraduates, and lots and lots of soda.

AND Gate 

   
 


# Different Types of Switches


Mechanical Switch

 

Electro-mechanical Relay

  


Fluid Pressure Valve

 


Electronic Tube

Called a "valve" in England

 

Transistor

 


# Logic Gate Implementation


## using Transistors

Older style individual transistors


AND Gate

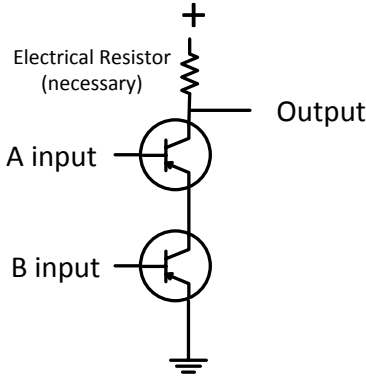


OR Gate

 


NOT Gate

 

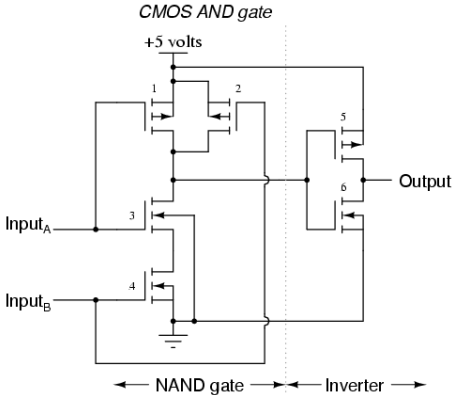
CMOS type transistors eliminate the need for resistors, allowing millions of transistors on a single chip



CMOS OR gate





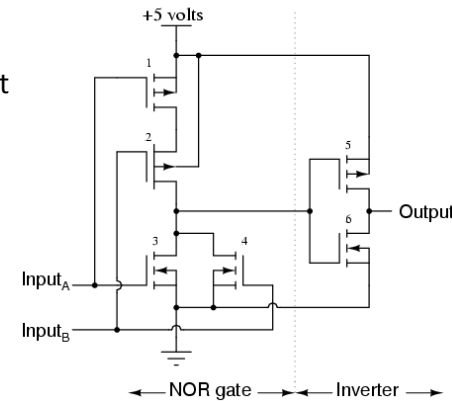


+5 volts





 


# Logic Gate Implementation






## XOR Gate

     

## NAND Gate

     


## NOR Gate

     


# NAND can implement all other logic gates


AND Gate

 


OR Gate

 


NOT Gate

 

XOR Gate

 

NOR Gate

 

**Next Presentation:  
Full Adder and Five Bit Adder**