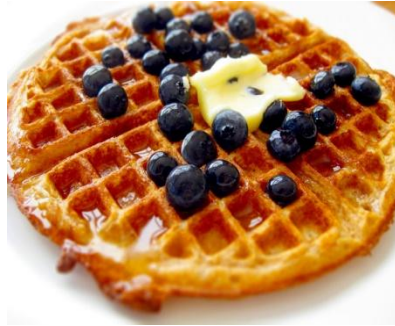


Simple Logic



The only purpose of a waffle is to get the maple syrup and butter into my mouth.

One morning I was really hungry and made both of these:



Blueberry Waffle



Pecan Waffle

I did not make either of these:




Pork and Kale Waffle



Masala Waffle

NOT logic

Did I **NOT** make a:

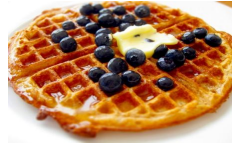

Blueberry Waffle

?

NOT logic

I did NOT make a:




Blueberry Waffle

False

NOT logic

I did **NOT** make a:

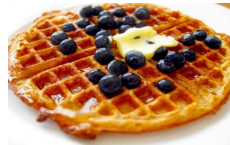

Blueberry Waffle

False

Did I **NOT** make a:




Pork and
Kale Waffle

?

NOT logic

I did NOT make a:

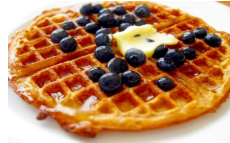

Blueberry Waffle

False

I did NOT make a:



Pork and
Kale Waffle


True

NOT logic

NOT True is False

NOT False is True

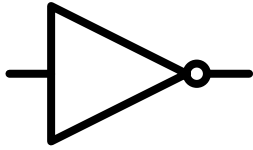Applying NOT to a statement flips its truth or falsity.



NOT Truth Table

NOT

0	1
1	0

NOT 0 is 1 (the negative of a false statement is a true statement)

NOT 1 is 0 (the negative of a true statement is a false statement)



A NOT Gate is like a light switch in a room that has been turned upside down. When you flip it up, normally turning it on, the light goes off. When you flip it down, normally turning it off, the light goes on.

Logic Gate Implementation

NOT Gate




NOT closed is open
NOT 1 = 0



NOT open is closed
NOT 0 = 1

AND logic

Did I make a:

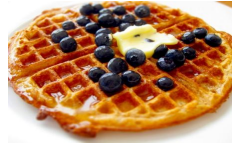

Blueberry Waffle

AND




Pecan Waffle

?

AND logic

I made a:

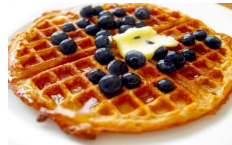

Blueberry Waffle

AND




Pecan Waffle

True

AND logic

I made a:

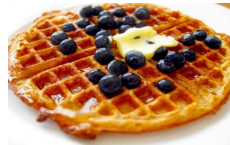

Blueberry Waffle

AND



Pecan Waffle

True

Did I make a:



Blueberry Waffle

AND




Masala Waffle

?

AND logic

I made a:

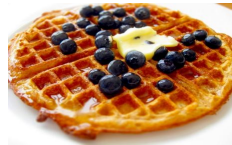

Blueberry Waffle

AND



Pecan Waffle

True

I made a:



Blueberry Waffle

AND




Masala Waffle

False

AND logic

I made a:

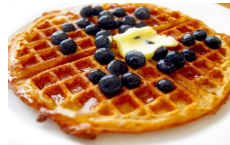

Blueberry Waffle

AND



Pecan Waffle

True

I made a:



Blueberry Waffle

AND



Masala Waffle

False

Did I make a:



Pork and
Kale Waffle

AND




Pecan Waffle

?

AND logic

I made a:

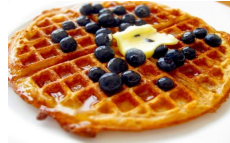

Blueberry Waffle

AND



Pecan Waffle

True

I made a:



Blueberry Waffle

AND



Masala Waffle

False

I made a:



Pork and
Kale Waffle

AND




Pecan Waffle

False

AND logic

I made a:

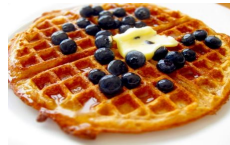

Blueberry Waffle

AND



Pecan Waffle

True

I made a:



Blueberry Waffle

AND



Masala Waffle

False

I made a:



Pork and
Kale Waffle

AND



Pecan Waffle

False

Did I make a:



Pork and
Kale Waffle

AND




Masala Waffle

?

AND logic

I made a:

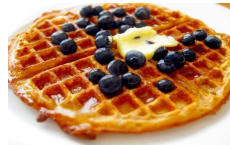

Blueberry Waffle

AND



Pecan Waffle

True

I made a:



Blueberry Waffle

AND



Masala Waffle

False

I made a:



Pork and
Kale Waffle

AND



Pecan Waffle

False

I made a:



Pork and
Kale Waffle

AND



Masala Waffle

False


AND logic

True AND True = True

True AND False = False

False AND True = False

False AND False = False

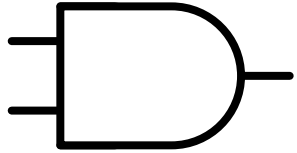

AND Truth Table


AND	0	1
0	0	0
1	0	1





- 0 AND 0 is 0 (a false statement AND a false statement is a false combination)
- 0 AND 1 is 0 (a false statement AND a true statement is a false combination)
- 1 AND 0 is 0 (a true statement AND a false statement is a false combination)
- 1 AND 1 is 1 (a true statement AND a true statement is a true combination)



An AND Gate is two similar to draw bridges in a row. If either one is up, then you won't be able to drive through.


Logic Gate Implementation

AND Gate 

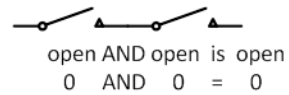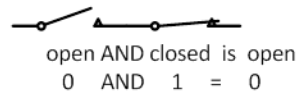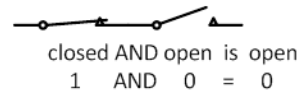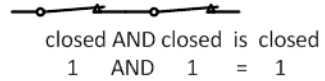

OR logic

Did I make a:

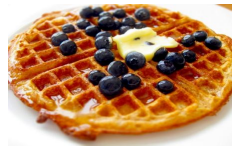

Blueberry Waffle

OR




Masala Waffle

?

OR logic

I made a:

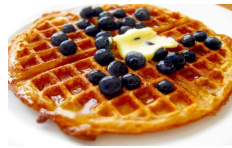

Blueberry Waffle

OR




Masala Waffle

True

OR logic

I made a:

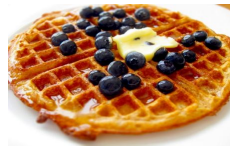

Blueberry Waffle

OR



Masala Waffle

True

Did I make a:



Pork and
Kale Waffle

OR




Pecan Waffle

?

OR logic

I made a:

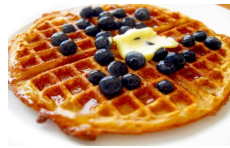

Blueberry Waffle

OR



Masala Waffle

True

I made a:



Pork and
Kale Waffle

OR




Pecan Waffle

True

OR logic

I made a:

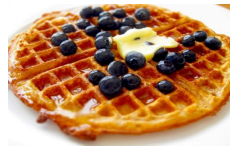

Blueberry Waffle

OR



Masala Waffle

True

I made a:



Pork and Kale Waffle

OR



Pecan Waffle

True

Did I make a:



Pork and Kale Waffle

OR




Masala Waffle

?

OR logic

I made a:

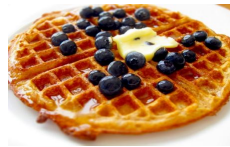

Blueberry Waffle

OR



Masala Waffle

True

I made a:



Pork and
Kale Waffle

OR



Pecan Waffle

True

I made a:



Pork and
Kale Waffle

OR




Masala Waffle

False

OR logic

Did I make a:

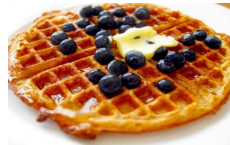

Blueberry Waffle

OR



Pecan Waffle

?

I made a:



Blueberry Waffle

OR



Masala Waffle

True

I made a:



Pork and
Kale Waffle

OR



Pecan Waffle

True

I made a:



Pork and
Kale Waffle

OR




Masala Waffle

False

OR logic

I made a:

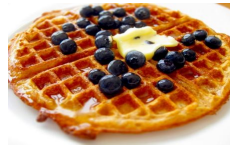

Blueberry Waffle

OR



Pecan Waffle

True

I made a:



Blueberry Waffle

OR



Masala Waffle

True

I made a:



Pork and Kale Waffle

OR



Pecan Waffle

True

I made a:



Pork and Kale Waffle

OR



Masala Waffle

False


OR logic

True OR True = True

True OR False = True

False OR True = True

False OR False = False

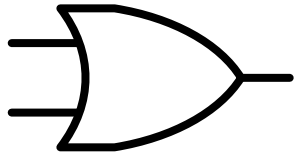

OR Truth Table

Inclusive OR

OR	0	1
0	0	1
1	1	1


- 0 OR 0 is 0 (a false statement OR a false statement is a false combination)
- 0 OR 1 is 1 (a false statement OR a true statement is a true combination)
- 1 OR 0 is 1 (a true statement OR a false statement is a true combination)
- 1 OR 1 is 1 (a true statement OR a true statement is a true combination)




An OR Gate is two similar to draw bridges in parallel. If either one is down, you will be able to drive through.

Logic Gate Implementation


OR Gate

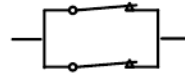

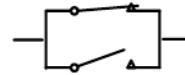
closed OR closed is closed
 $1 \text{ OR } 1 = 1$



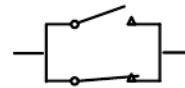closed OR open is closed
 $1 \text{ OR } 0 = 1$



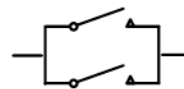
open OR closed is closed
 $0 \text{ OR } 1 = 1$




open OR open is open
 $0 \text{ OR } 0 = 0$

Logic Gate Implementation

To make a computer, all you need is Memorial Stadium for an afternoon, a few thousand chairs, a few thousand undergraduates, one pizza for each three undergraduates, and lots and lots of soda.

AND Gate 

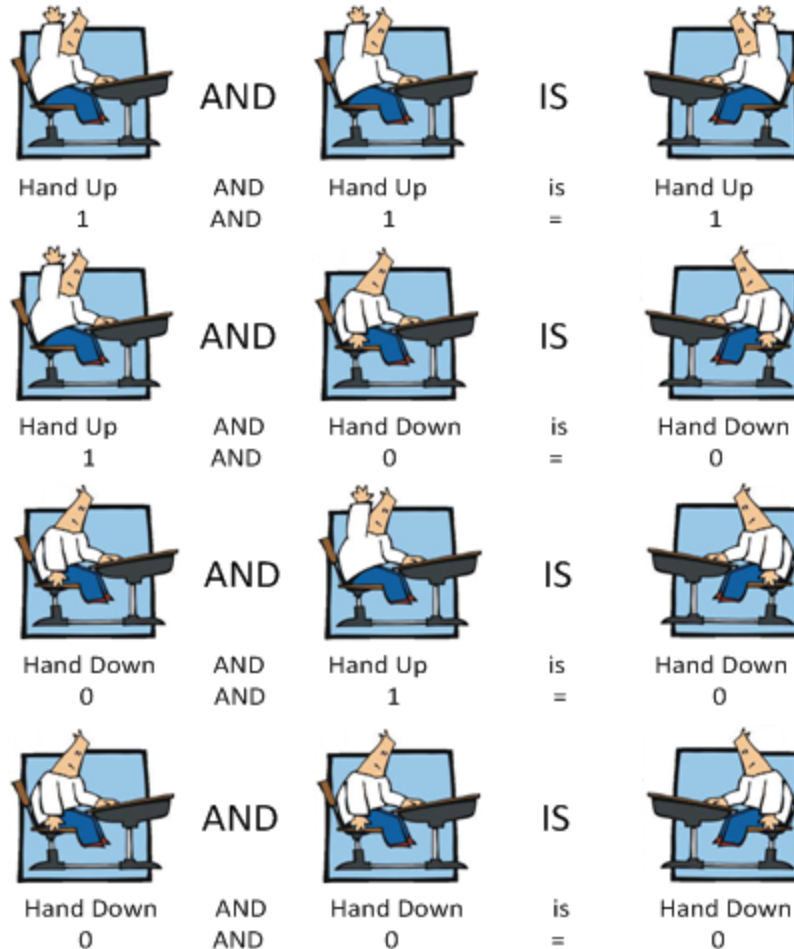


Different Types of Switches


Mechanical Switch



Electro-mechanical Relay

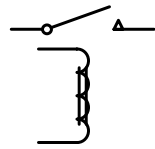


Fluid Pressure Valve

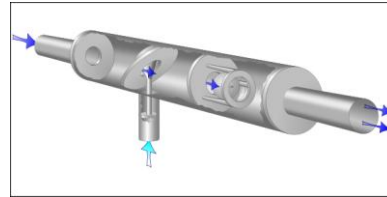


Electronic Tube

Called a "valve" in England

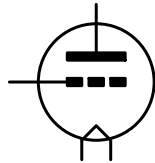


Transistor

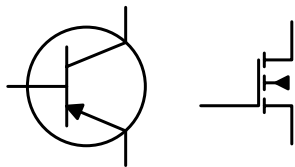


Logic Gate Implementation

using Transistors


AND Gate

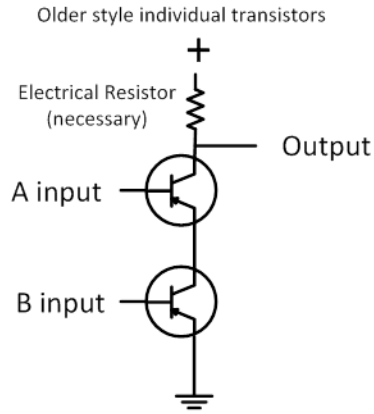




OR Gate

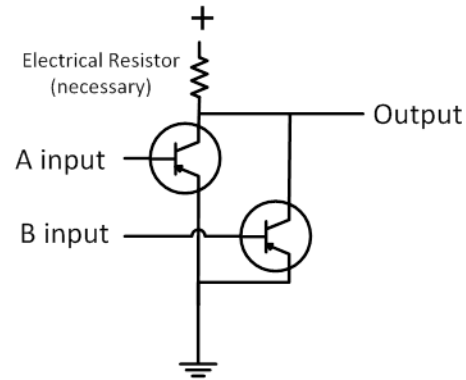

NOT Gate

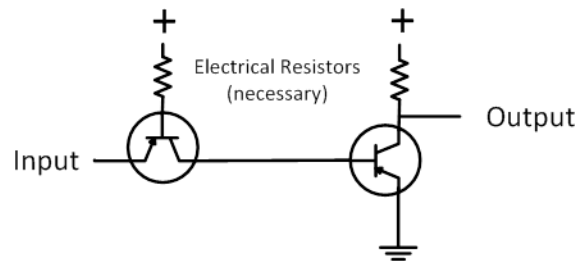



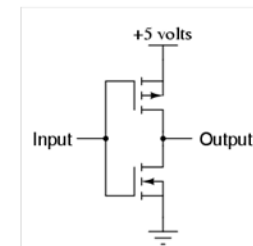
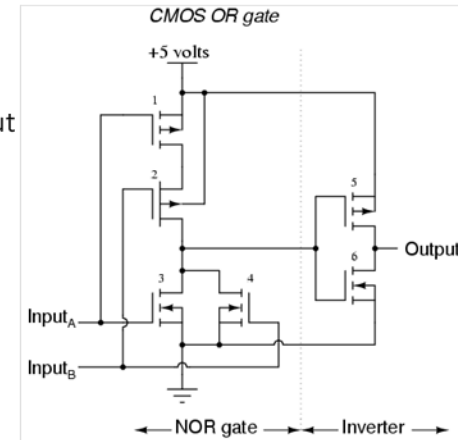
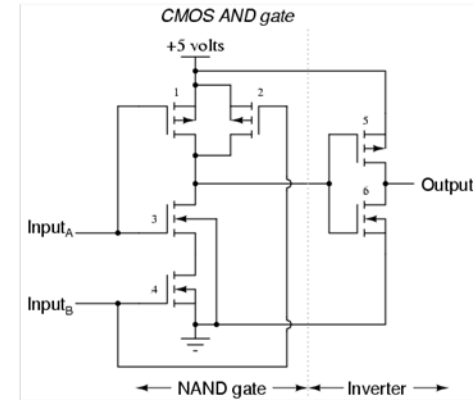
CMOS type transistors eliminate the need for resistors, allowing millions of transistors on a single chip



Exclusive OR Gate (XOR)

Outputs True if either input is True, but not if both inputs are True

XOR Gate

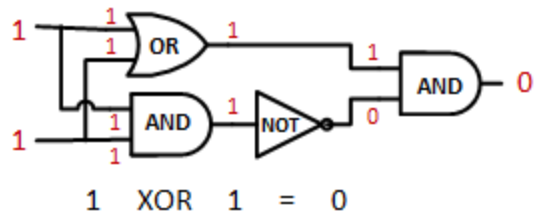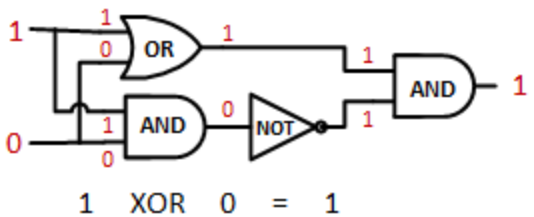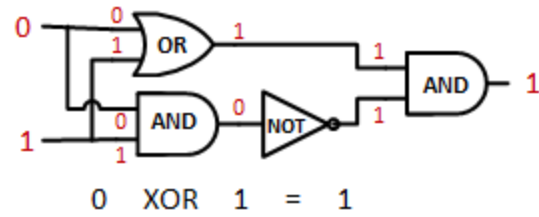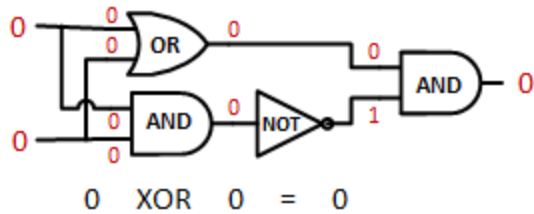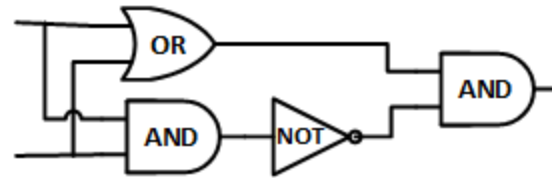

From Page 379 of Principia Mathematica
by Bertrand Russell and Alfred North Whitehead, 1910 - 1913

***54·43.** $\vdash \therefore \alpha, \beta \in 1 \supset : \alpha \cap \beta = \Lambda \equiv \alpha \cup \beta \in 2$

Dem.

$\vdash \cdot *54\cdot26 \supset \vdash \therefore \alpha = \iota'x \cdot \beta = \iota'y \supset : \alpha \cup \beta \in 2 \equiv \cdot x \neq y \cdot$

[*51·231] $\equiv \cdot \iota'x \cap \iota'y = \Lambda \cdot$

[*13·12] $\equiv \cdot \alpha \cap \beta = \Lambda$ (1)


$\vdash \cdot (1) \cdot *11\cdot11\cdot35 \supset$

$\vdash \therefore (\exists x, y) \cdot \alpha = \iota'x \cdot \beta = \iota'y \supset : \alpha \cup \beta \in 2 \equiv \cdot \alpha \cap \beta = \Lambda$ (2)


$\vdash \cdot (2) \cdot *11\cdot54 \cdot *52\cdot1 \supset \vdash \cdot \text{Prop}$

From this proposition it will follow, when arithmetical addition has been defined, that $1 + 1 = 2$.

Five Bit Adder

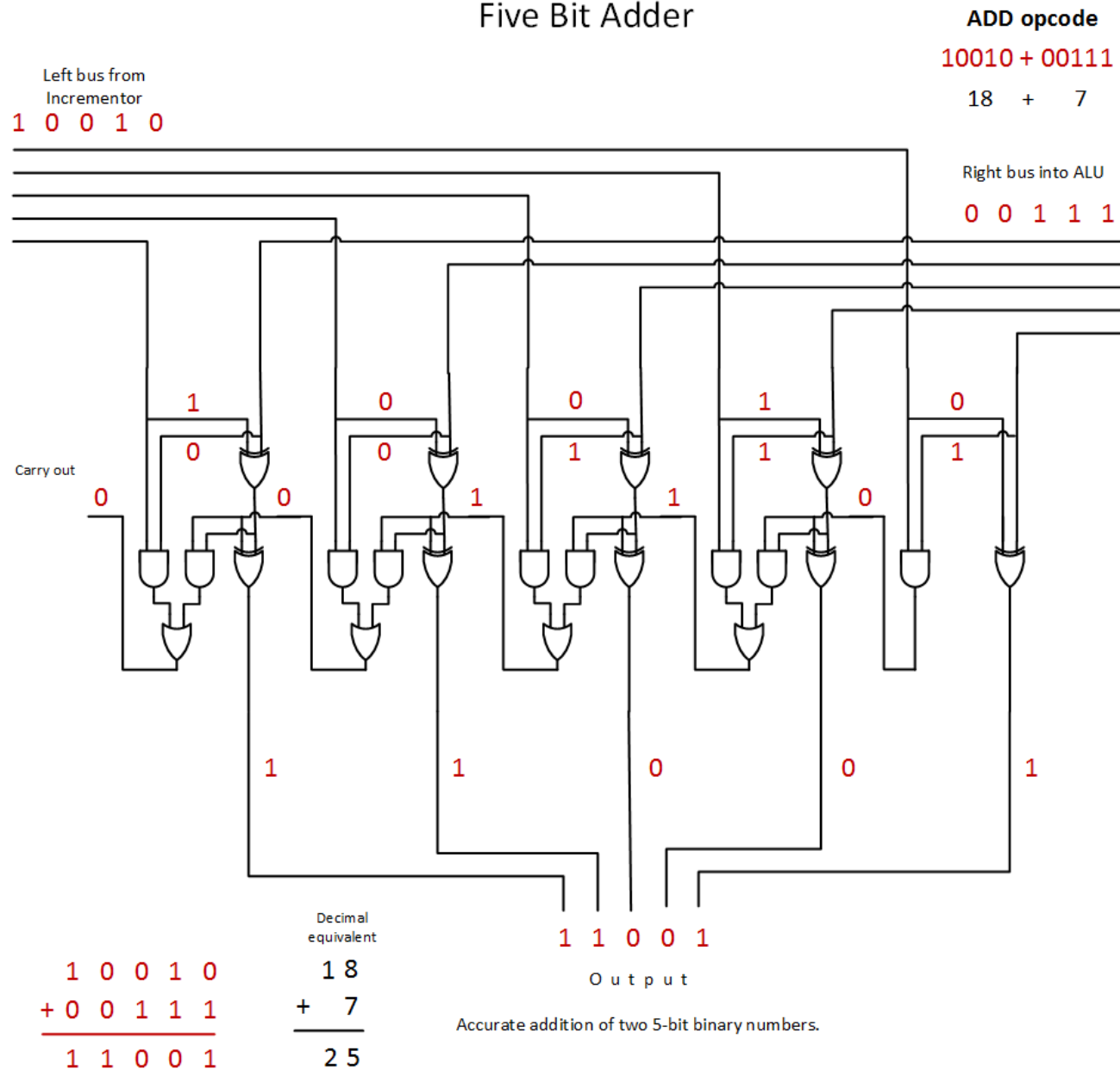


Twos Complementor

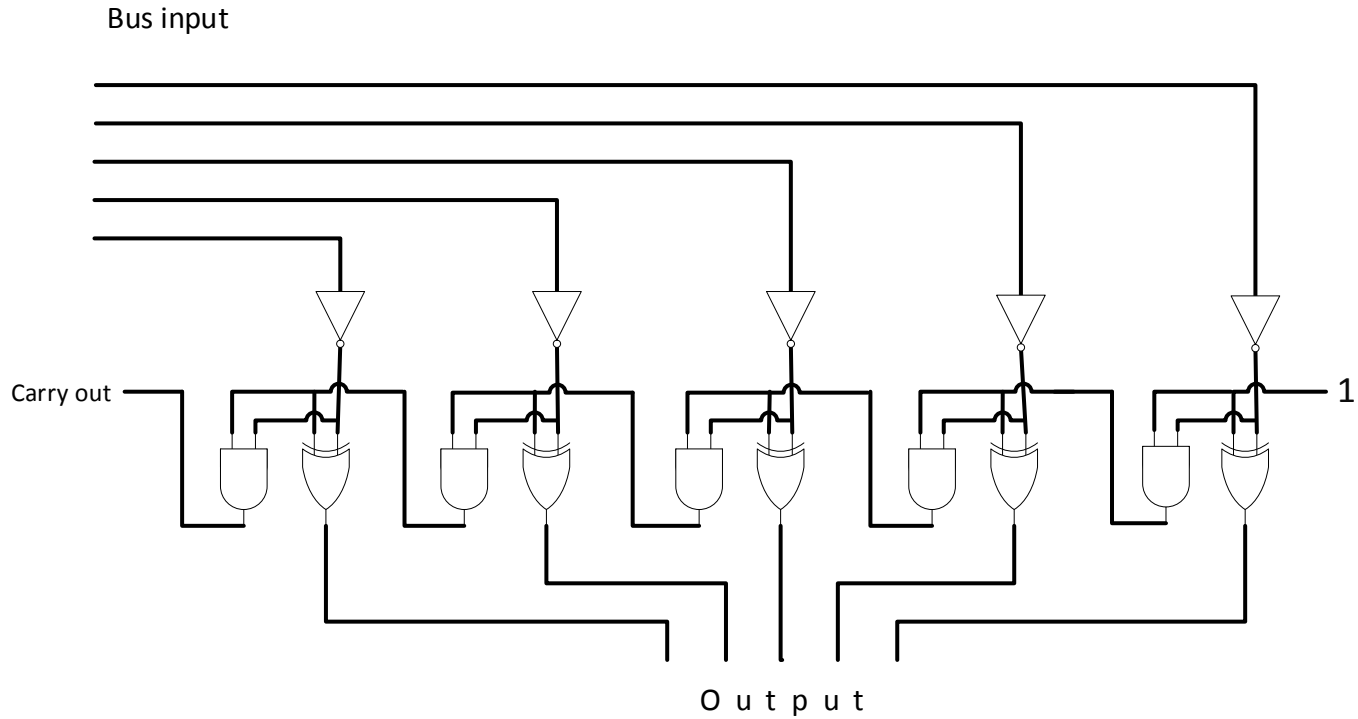

twos complement of the input bus

Five Bit Adder

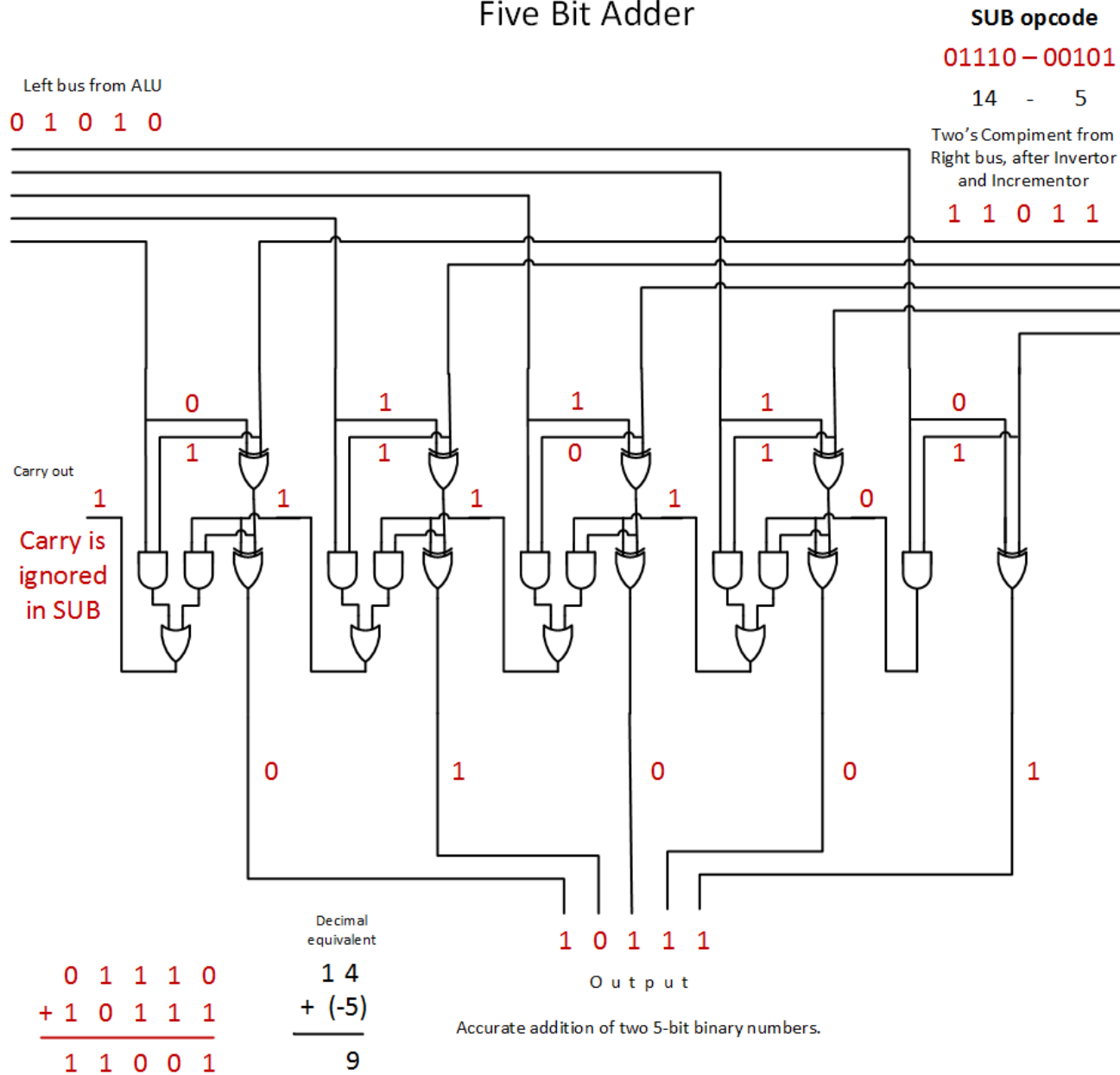

Multiplication and Division

Multiplication and division is done in hardware by various logic gate designs. Typically, modern computers use about 4000 gates to multiply or divide two 64-bit binary numbers. This is the meaning of a “64-bit” computer. 4000 gates is minuscule compared to the approximately half billion gates on a typical modern Central Processing Unit (CPU) chip.

End of Presentation